

Aula 13 - Exercise Class 4

Prof. Marcelino Andrade

Faculdade UnB Gama

June 5, 2017

Contents

CHAPTER 7 First-Order Circuits


CHAPTER 8 Second-Order Circuits

CHAPTER 16 Applications of the Laplace Transform

Introduction to Electric Circuits by James A. Svoboda, Richard C. Dorf, 9th Edition

First-Order Circuit RL

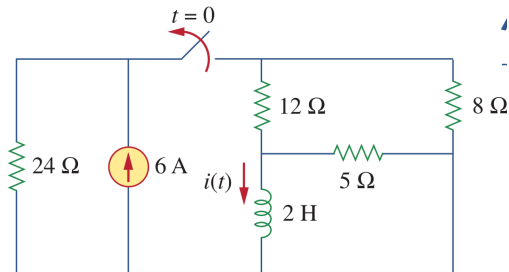
Practice Problem 7.4 - For the circuit in Fig. below, find $i(t)$ for $t > 0$.



Answer: $2e^{-2t}$ A, $t > 0$.

Step Response of an First-Order Circuit

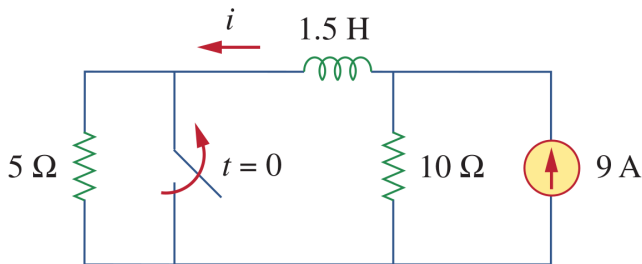
Practice Problem 7.12 - The switch in Fig. below has been closed for a long time. It opens at $t = 0$. Find $i(t)$ for $t > 0$.



Answer: $i(t) = 6 + 3e^{-10t}\text{ A}$ for all $t > 0$.

Circuit Theorems

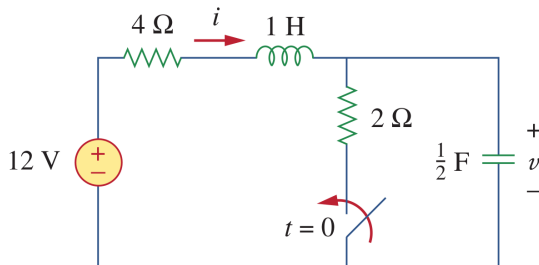
Example 8.9 - Find the complete response v and then i for $t > 0$ in the circuit of Fig. below.



Answer: $v(t) = 4 + 12e^{-2t} - 4e^{-3t}$ V, $t > 0$

Circuit Element Models

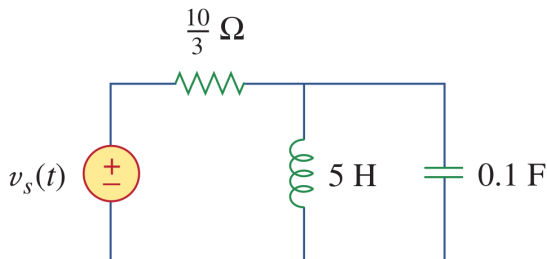
Example 16.4 - Consider the circuit in Fig. below. Find the value of the voltage across the capacitor assuming that the value of $v_s(t) = 10u(t)$ V and assume that at $t = 0$, -1 A flows through the inductor and +5 V is across the capacitor.



Answer: $v_c(t) = (35e^{-t} - 30e^{-2t})u(t)$

Transfer Functions

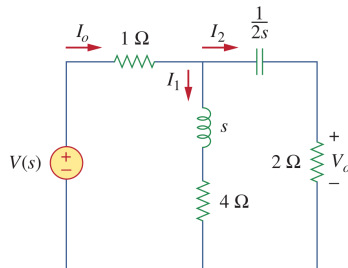Problem 7.8-6 - Determine the transfer function $H(s) = \frac{I_1(s)}{I_o(s)}$ of the circuit in Fig. below.



Answer: $H(s) = \frac{4s + 1}{2s^2 + 12s + 1}$