

# Aula 2: Methods of Analysis of Resistive Circuits (Node Voltage)

Prof. Marcelino Andrade

Faculdade UnB Gama

10 de agosto de 2017

# Contents

Introduction (4.1)

Node Voltage Analysis of Circuits with Current Sources (4.2)

Node Voltage Analysis of Circuits with Current and Voltage Sources (4.3)

Node Voltage Analysis with Dependent Sources (4.4)

Circuit Analysis Using MATLAB (4.9)

Introduction to Electric Circuits 9th Edition by James A. Svoboda, Richard C. Dorf




## Introduction

In this chapter, we consider two methods for writing a smaller set of simultaneous equations:

- ♣ The node voltage method.
- ♣ The mesh current method.


To analyze an electric circuit, we write and solve a set of equations. We apply Kirchhoff's current and voltage laws to get some of the equations. This method works well for small circuits, but the set of equations can get quite large for even moderate-sized circuits.
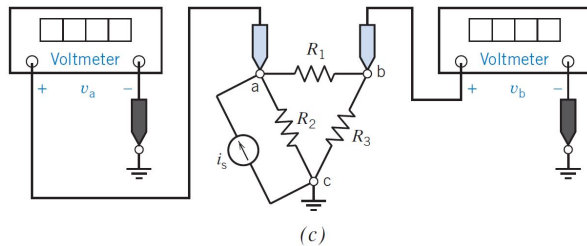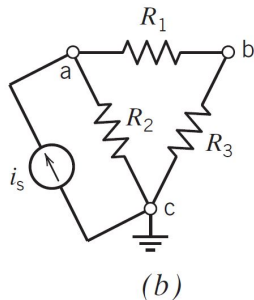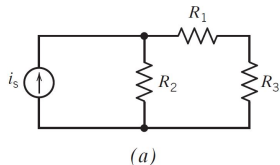
## Node Voltage Analysis of Circuits with Current Sources




- (a) A circuit with three nodes.
- (b) The circuit with nodes labeled and reference node marked.
- (c) Using voltmeters to measure the node voltages.

## The Node Voltage

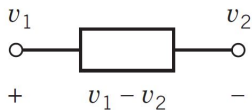


(a)

Generic element

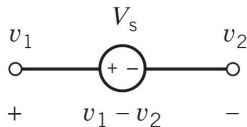

(b)


Voltage source

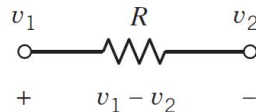

(c)

Resistor

## The Node Equations

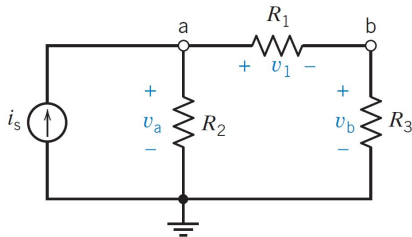


To write a set of node equations, we do two things:

- ♣ Express element currents as functions of the node voltages.
- ♣ Apply Kirchhoff's current law (KCL) at each of the nodes of the circuit except for the reference node.

## Node Voltage Analysis

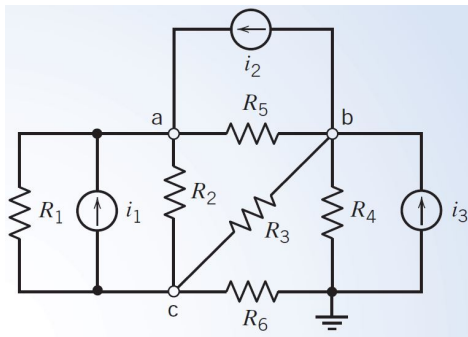
**EXAMPLE 4.2-2** - Obtain the node equations for the circuit.



$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} & -\frac{1}{R_5} & -(\frac{1}{R_1} + \frac{1}{R_2}) \\ -(\frac{1}{R_1} + \frac{1}{R_2}) & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} & -\frac{1}{R_3} \\ -\frac{1}{R_5} & -\frac{1}{R_3} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_6} \end{bmatrix} \times \begin{bmatrix} v_a \\ v_b \\ v_c \end{bmatrix} = \begin{bmatrix} i_1 + i_2 \\ i_3 - i_2 \\ -i_1 \end{bmatrix}$$

## Node Voltage Analysis

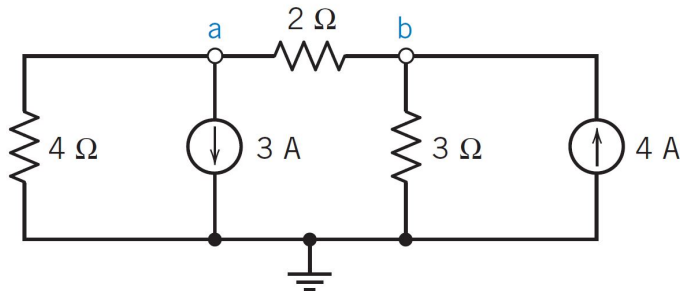**EXERCISE 4.2-2** - Determine the node voltages  $v_a$  and  $v_b$  for the circuit.




Answer:  $v_a = -4/3V$  and  $v_b = 4V$


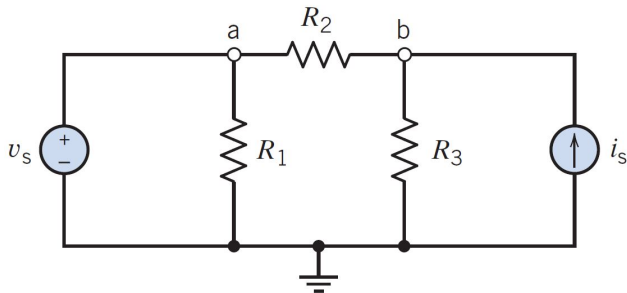
## Node Voltage Analysis of Circuits with Current and Voltage Sources

First we consider the circuit with a voltage source between ground and one of the other nodes.



$$v_a = v_s \quad (1)$$


$$-i_s + \frac{v_b}{R_3} + \frac{v_b - v_a}{R_2} = 0 \quad (2)$$

$$-i_s + \frac{v_b}{R_3} + \frac{v_b - v_s}{R_2} = 0 \quad (3)$$

$$v_b = \frac{R_2 R_3 i_s + R_3 v_s}{R_2 + R_3} \quad (4)$$

## Node Equations

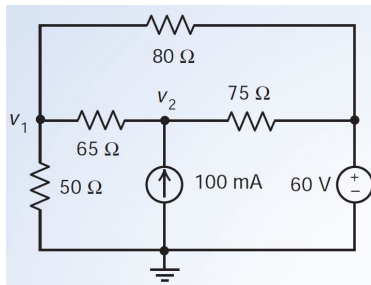**EXAMPLE 4.3-1** - Determine the values node voltages,  $v_1$  and  $v_2$ , in the circuit.




Answer:  $v_1 = 31.081V$  and  $v_2 = 47.990V$

## Node Voltage Analysis of Circuits with Supernode

Next, let us consider the circuit which includes a voltage source between two nodes.

Supernode

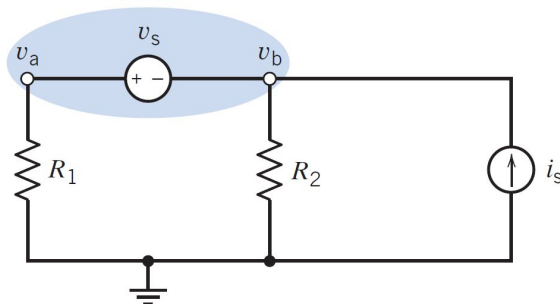

$$v_a - v_b = v_s \text{ or } v_a = v_s + v_b \quad (5)$$

$$-i_s + \frac{v_b}{R_2} + \frac{v_a}{R_1} = 0 \quad (6)$$


$$-i_s + \frac{v_b}{R_2} + \frac{v_s + v_b}{R_1} = 0 \quad (7)$$

$$v_b = \frac{R_1 R_2 i_s + R_2 v_s}{R_1 + R_2} \quad (8)$$

A supernode consists of two nodes connected by an independent or a dependent voltage source.

## Node Equations

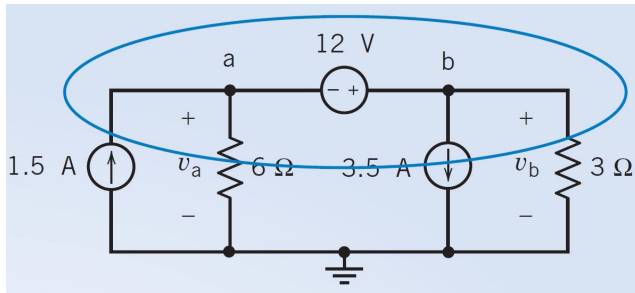
**EXAMPLE 4.3-2** - Determine the values of the node voltages  $v_a$  and  $v_b$  for the circuit.



Answer:  $v_a = -12V$  and  $v_b = 0V$

## Node Equations

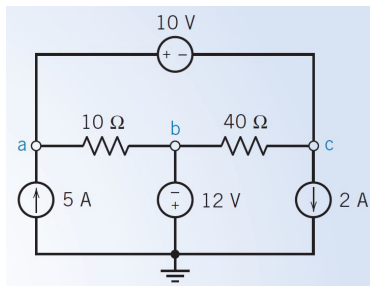
**EXAMPLE 4.3-3** - Determine the node voltages for the circuit shown.



Answer:  $v_a = 14V$   $v_b = -12V$  and  $v_c = 4V$

## Node Equations

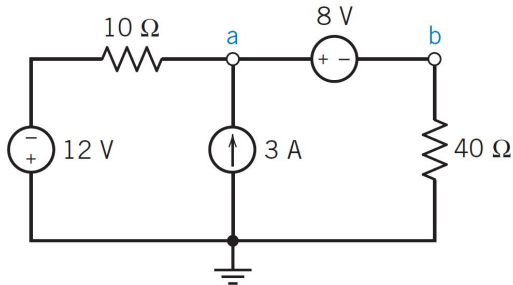
**EXERCISE 4.3-2** - Find the voltages  $v_a$  and  $v_b$  for the circuit.



Answer:  $v_a = 16V$  and  $v_b = 8V$
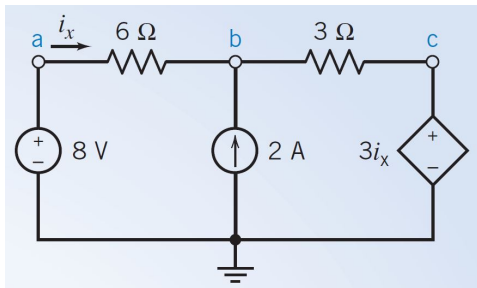
## Node Voltage Analysis with Dependent Sources

When a circuit contains a dependent source the controlling current or voltage of that dependent source must be expressed as a function of the node voltages.



$$i_x = \frac{v_a - v_b}{6} = \frac{8 - v_b}{6} \quad (9)$$

$$v_c = 3i_x = 3\left(\frac{8 - v_b}{6}\right) \quad (10)$$


$$-\frac{v_a - v_b}{6} - 2 - \frac{v_c - v_b}{3} = 0 \quad (11)$$

$$-\frac{8 - v_b}{6} - 2 - \frac{3\left(\frac{8 - v_b}{6}\right) - v_b}{3} = 0 \quad (12)$$

A supernode consists of two nodes connected by an independent or a dependent voltage source. Answer:  $v_a = 8V$ ,  $v_b = 7V$  and  $v_c = \frac{1}{2}V$

## Node Equations

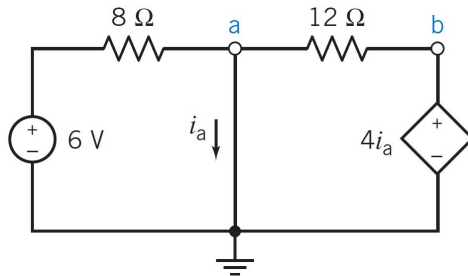**EXERCISE 4.4-1** - Find the node voltage  $v_b$  for the circuit shown.




Answer:  $v_b = 4.5V$


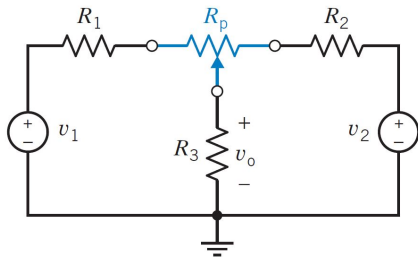
## Circuit Analysis Using MATLAB

In this section, we will use the MATLAB computer program to solve the equations.



We have seen that circuits that contain resistors and independent or dependent sources can be analyzed in the following way:

- ♣ Writing a set of node equations.
- ♣ Solving those equations simultaneously.

$$R_1 = 1000\Omega, R_2 = 1000\Omega, R_3 = 5000\Omega, v_1 = -v_2 = 15V \text{ and } R_p = 20.000\Omega$$