

Aula 9 - Exercise Class 3

Prof. Marcelino Andrade

Faculdade UnB Gama

April 24, 2017

Contents

CHAPTER 3 Resistive Circuits

CHAPTER 4 Methods of Analysis of Resistive Circuits

CHAPTER 5 Circuit Theorems


CHAPTER 6 The Operational Amplifier

CHAPTER 7 Energy Storage Elements

Introduction to Electric Circuits by James A. Svoboda, Richard C. Dorf, 9th Edition

Resistive Circuits

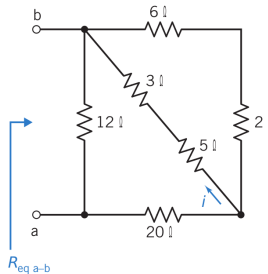
Problem 3.6-11 - Find i and $R_{eq\ a-b}$ if $v_{ab} = 40\text{ V}$ in the circuit of Figure below.



Answer: $i = \frac{5}{6}\text{ A}$ and $R_{eq\ a-b} = 8\Omega$.

Methods of Analysis of Resistive Circuits

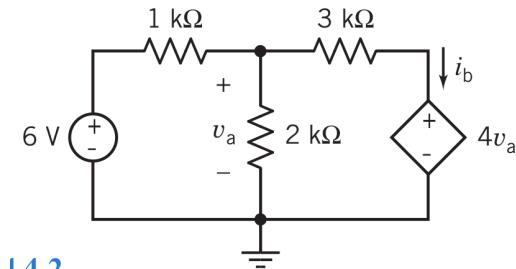Problem 4.4-2 - Find i_b for the circuit shown in Figure below.




14.2

Answer: $i_b = -12\text{mA}$.

Circuit Theorems

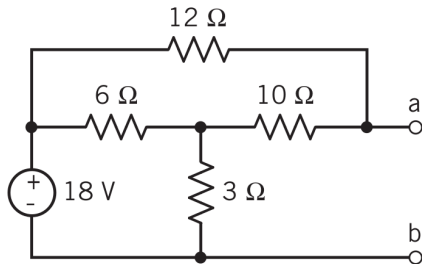
Problem 5.4-4 -Find the Thevenin equivalent circuit for the circuit shown in Figure below.



Answer: $v_t = 12V$ and $R_t = 6\Omega$

Operational Amplifier

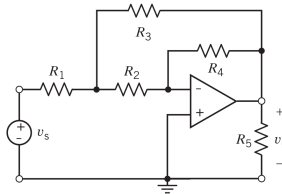
Problem 6.4-161 - The circuit shown in Figure below has one input, v_s , and one output, v_o . Express the gain $\frac{v_o}{v_s}$ in terms of the resistances R_1 , R_2 , R_3 , R_4 , and R_5 . Design the circuit so that $v_o = -20v_s$.



Answer: $\frac{v_o}{v_s} = \frac{-R_3 R_4}{R_1 R_2 + R_1 R_3 + R_2 R_3 + R_1 R_4}$ and $R_1 = 1\Omega$, $R_2 = 78\Omega$, $R_3 = 100\Omega$ e $R_4 = 2000\Omega$

Energy Storage Elements

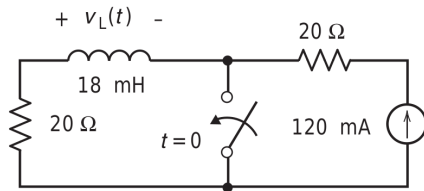Problem 7.8-6 - The switch in the circuit shown in Figure below has been open for a long time before it closes at time $t = 0$. Determine the values of $v_L(0^-)$, the voltage across the inductor immediately before the switch closes, and $v_L(0^+)$, the voltage across the inductor immediately after the switch closes.



Answer: $v_L(0^-) = 0V$ and $v_L(0^+) = 2.4V$