

Aula 4 - Exercise Class 1

Prof. Marcelino Andrade

Faculdade UnB Gama

March 28, 2017

Contents

Kirchhoff's Laws (2.4)

Voltage Division (2.5) and Current Division (2.6)


Nodal Analysis (3.2)

Mesh Analysis (3.4)

Fundamentals of Electric Circuits (Alexander and Sadiku), 4th Edition

Kirchhoff's Laws

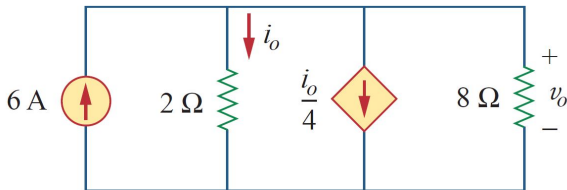
Practice Problem 2.7 - Find v_0 and i_0 in the circuit.



Answer: $i_0 = 4A$ and $v_0 = 8V$

Kirchhoff's Laws

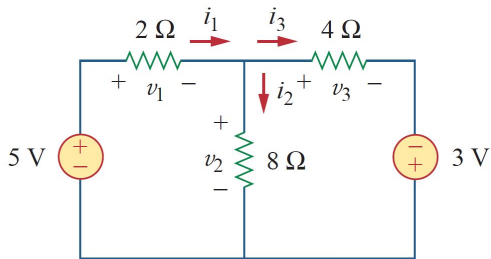
Practice Problem 2.8 - Find the currents and voltages in the circuit shown.



Answer: $v_1 = 3V$, $v_2 = 2V$, $v_3 = 5V$, $i_1 = 1.5A$, $i_2 = 0.25A$ and $i_3 = 1.25V$

Voltage Division and Current Division

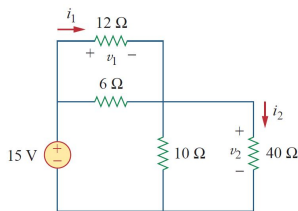
Practice Problem 2.12 - Find v_1 and v_2 in the circuit shown. Also calculate i_1 and i_2 the power dissipated in the 12Ω and 40Ω resistors.



Answer: $v_1 = 5V$, $i_1 = 416.7mA$, $p_1 = 2.083W$, $v_2 = 10V$, $i_2 = 250mA$ and $p_2 = 2.5W$


Equivalent Resistance

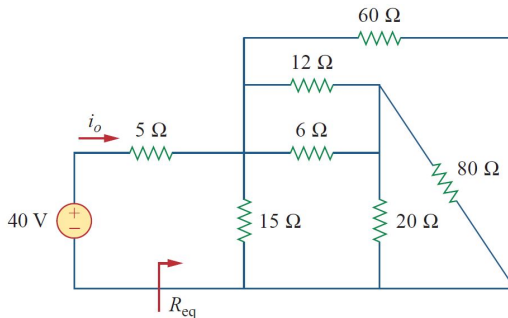Problem 2.38 - Find R_{eq} and i_o in the circuit.



Nodal Analysis

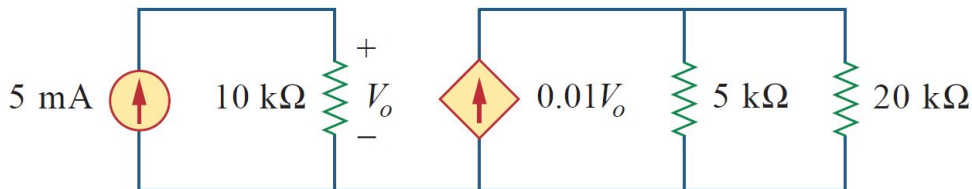
Problem 2.25 - For the network, find the current, voltage, and power associated with the 20-k Ω resistor.



Answer: $i = 0.1A$, $v = 2kV$, and $p = 0.2kW$

Nodal Analysis

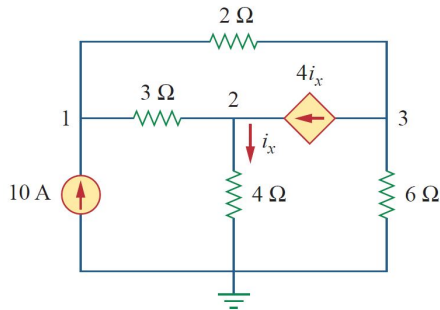
Practice Problem 3.2 - Find the voltages at the three nonreference nodes in the circuit.



Answer: $v_1 = 80V$, $v_2 = -64V$, and $v_3 = 156V$

Nodal Analysis

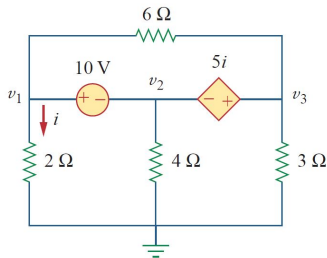
Practice Problem 3.4 - Find v_1 , v_2 and v_3 in the circuit using nodal analysis.



Answer: $v_1 = 3.043V$, $v_2 = -6.956V$, and $v_3 = 0.6522V$

Mesh Analysis



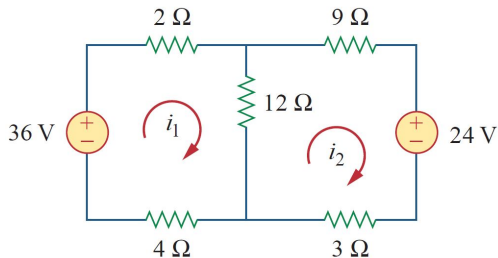
Practice Problem 3.5 - Calculate the mesh currents and of the circuit.



Answer: $i_1 = 2A$ and $i_2 = 0A$

Mesh Analysis

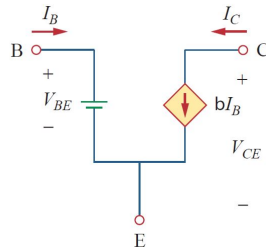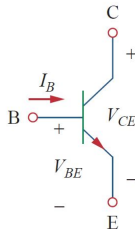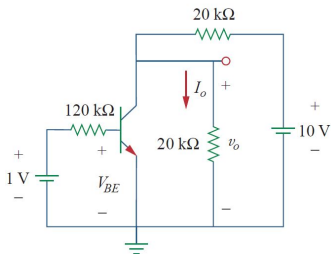
Practice Problem 3.13 -The transistor circuit has $\beta = 80$ and $v_{BE} = 0.7V$. Find v_o and i_o .



Answer: $v_o = 3V$ and $i_o = 150\mu A$

Mesh Analysis

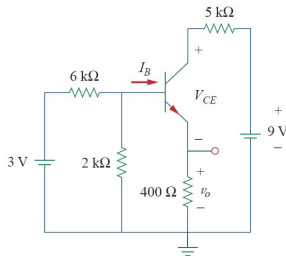Problem 3.91 - For the transistor circuit, find I_B , V_{CE} and v_o . Take $\beta = 200$ and $V_{BE} = 0.7V$.



Answer: $v_B = 0.61\text{mA}$, $V_{CE} = 8.34V$ and $v_o = 49\text{mV}$